

# Felix\_Chen\_Lab4

Tags


## Part 1

### DRAM

#### The hspice file

```
Lab4 > DRAM.sp
1  ** Simple DRAM using PTM 45 nm Node
2
3  .include CMOSP.inc
4  .include CMOSN.inc
5
6  .PARAM VDD = 0.8
7
8  ** Circuit Netlist
9
10 ** Supply and Input Sources
11 VSUP X 0 'VDD/2'
12 VG Y 0 0
13
14 ** Transistors
15 M1 Z Y X VDD CMOSN L=45n W=120n
16
17 ** Capacitor
18 C1 Z 0 C=10f
19
20 ** Initial condition
21 .IC V(Z) = 'VDD'
22
23 ** Analysis Setup
24 .TRAN 0.001u 800u
25
26 ** Control Information
27 .OPTION POST BRIEF NOMOD PROBE MEASOUT
28
29 ** Print and Measurement
30 .PRINT V(X) V(Z)
31 .MEASURE TRAN RTL TRIG AT=0 TARG V(Z) VAL=0.6 FALL=1
32 .MEASURE TRAN AVG_CUR AVG I(C1) FROM 0 to 'RTL'
33 .MEASURE TRAN AVG_PWR AVG P(C1) FROM 0 to 'RTL'
34
35 .END
```

**C=0.1fF**

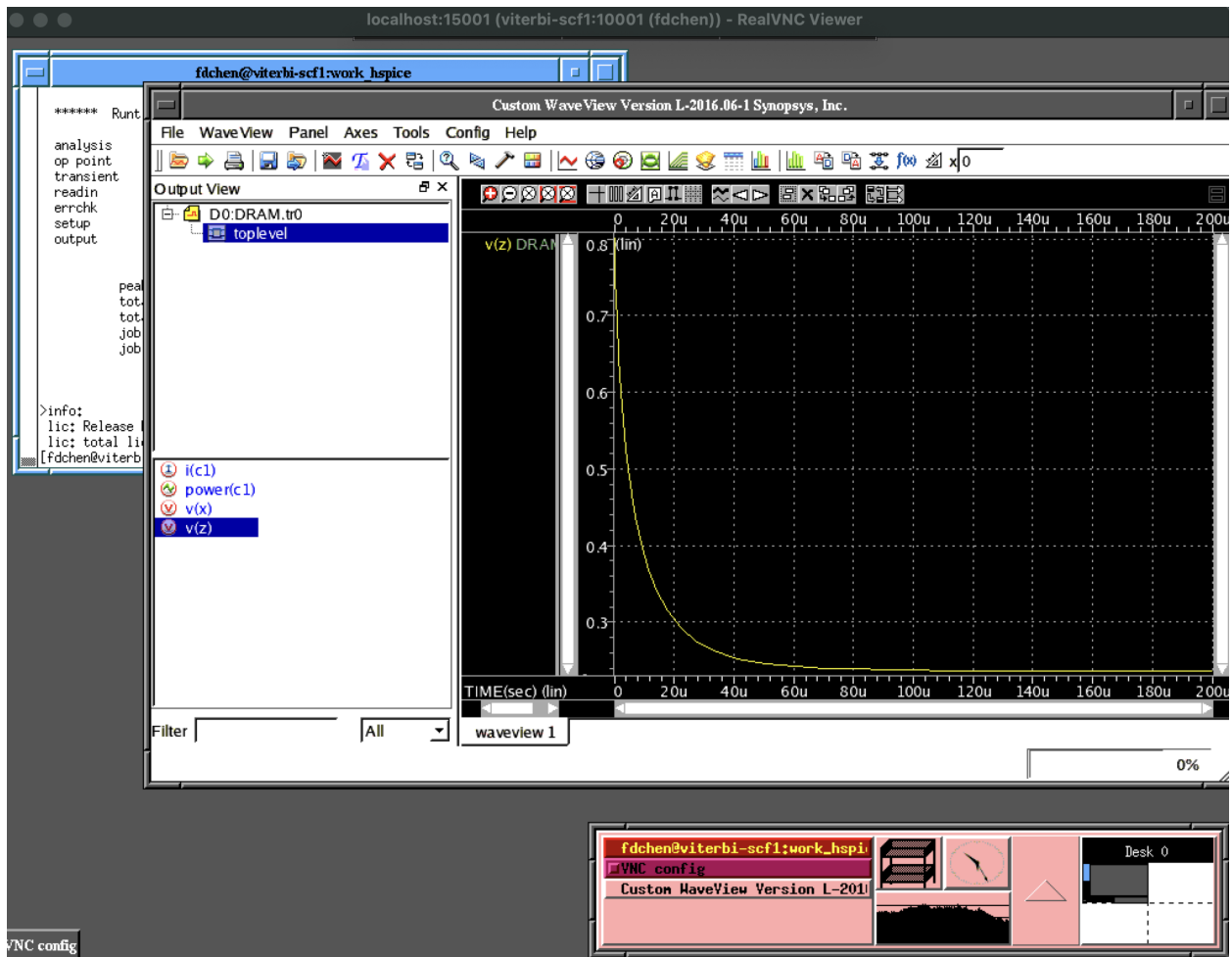


$$RTL = 2.151e^{-6}$$

$$\text{average power} = -6.546e^{-12}$$

$$\text{average current} = -9.342e^{-12}$$

$$C=1fF$$

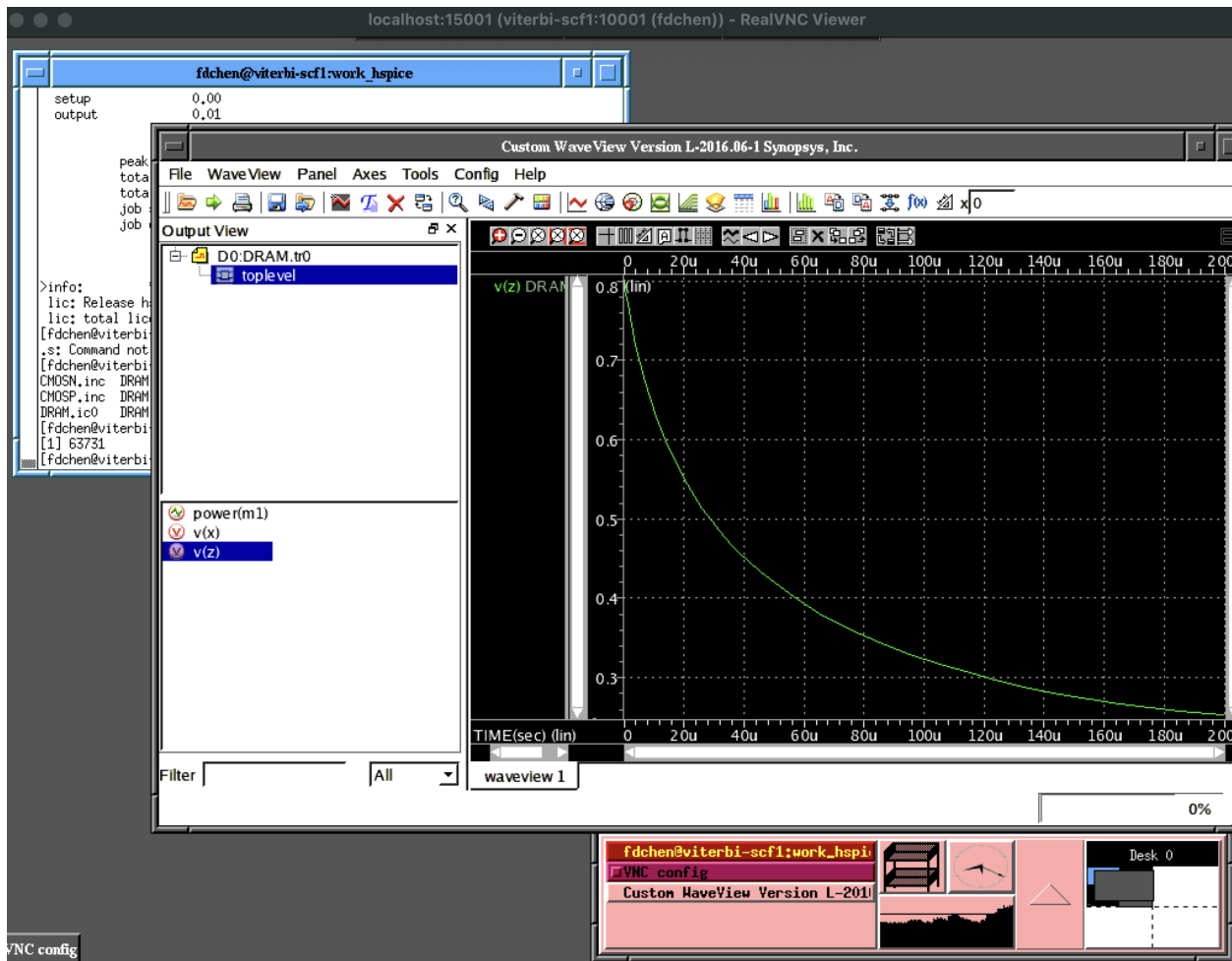


$$RTL = 1.370e^{-5}$$

$$\text{average power} = -1.024e^{-11}$$

$$\text{average current} = -1.457e^{-11}$$

$$C=10fF$$

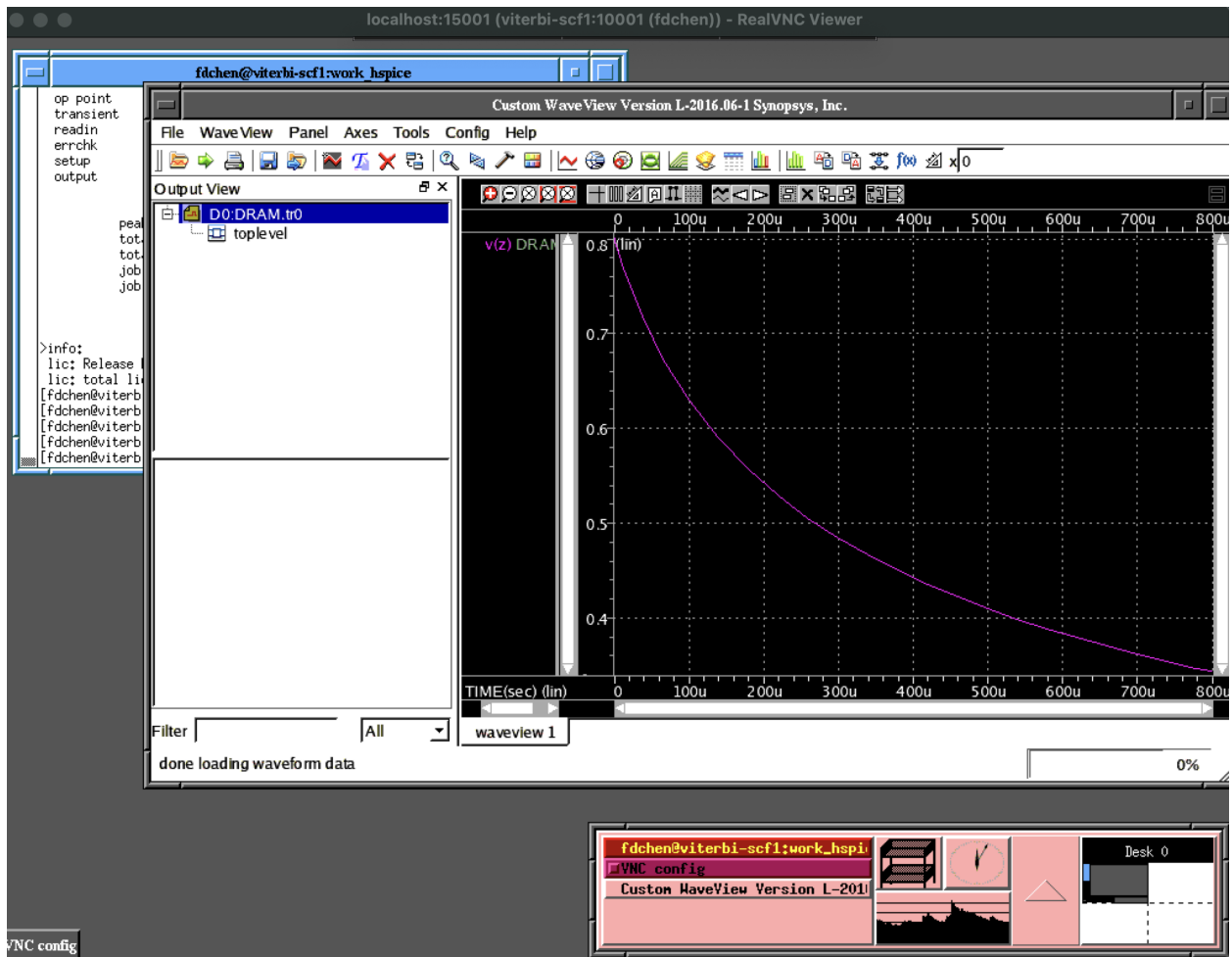

$$RTL = 1.29e^{-4}$$

$$\text{average power} = -1.093e^{-11}$$


$$\text{average current} = -1.557e^{-11}$$

## Observation

The higher the capacitance of the capacitor is, the longer it takes to discharge. This makes sense because capacitors with the most capacitance holds the most charge for the same voltage.

## NAND2

Waveform

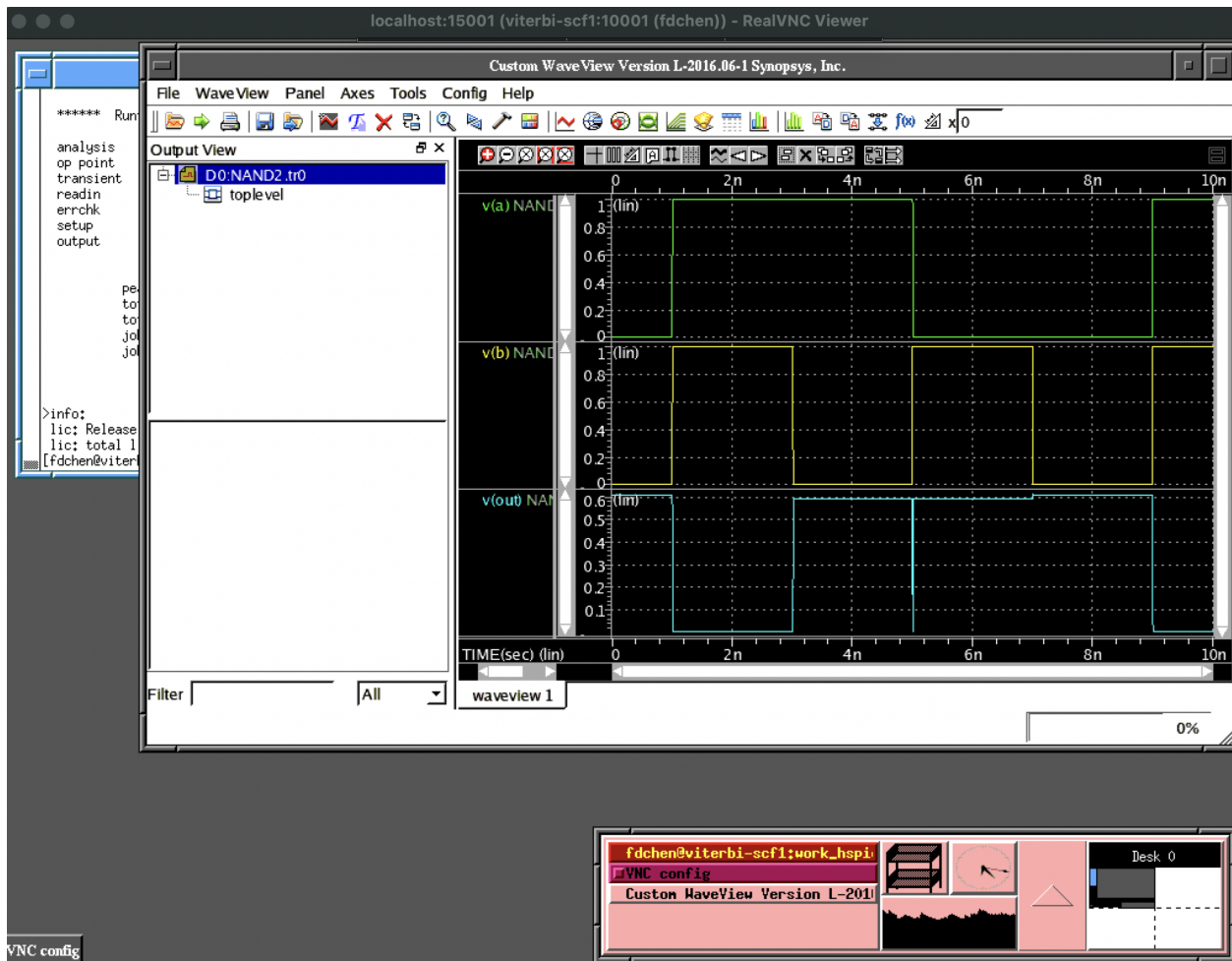

File

```
CMOSN.inc  DRAM.sp  NAND2.sp x  inverter.sp  RC.sp
Lab4 > NAND2.sp
1  ** Simple DRAM using PTM 45 nm Node
2
3  .include CMOSP.inc
4  .include CMOSN.inc
5
6  ** Circuit Netlist
7
8  ** Supply and Input Sources
9  V_SUP VDD 0 1
10 VPIN_A A 0 PULSE 0 1.0 1ns 10ps 10ps 4ns 8ns
11 VPIN_B B 0 PULSE 0 1.0 1ns 10ps 10ps 2ns 4ns
12
13 ** Transistors
14 M_PU_A OUT A VDD CMOSP L=45n W=180n
15 M_PU_B OUT B VDD CMOSP L=45n W=180n
16
17 M_PD_A OUT A X CMOSN L=45n W=240n
18 M_PD_B X B 0 CMOSN L=45n W=240n
19
20 ** Initial condition
21 .IC V(X) = 0
22
23 ** Analysis Setup
24 .TRAN 0.1ns 10n
25
26 ** Control Information
27 .OPTION POST BRIEF NOMOD PROBE MEASOUT
28
29 ** Print and Measurement
30 .PRINT V(A) V(B) V(OUT)
31
32 .END
```

## Part 2

### DRAM.sp

```
DRAM.sp × NAND2.sp generate_input.py organize_output.py M README.md U ou
Lab4 > DRAM.sp
1  ** Simple DRAM using PTM 45 nm Node
2
3  .include CMOSP.inc
4  .include CMOSN.inc
5  .include input_data.txt
6
7  .PARAM VDD = 0.8
8
9  ** Circuit Netlist
10
11  ** Supply and Input Sources
12  VSUP X 0 'VDD/2'
13  VG Y 0 0
14
15  ** Transistors
16  M1 Z Y X VDD CMOSN L=45n W=120n
17
18  ** Capacitor
19  C1 Z 0 C=10f
20
21  ** Initial condition
22  .IC V(Z) = 'VDD'
23
24  ** Analysis Setup
25  .TRAN 1u 200u sweep data = mydata
26
27  ** Control Information
28  .OPTION POST BRIEF NOMOD PROBE MEASOUT
29
30  ** Print and Measurement
31  .PRINT V(X) V(Z)
32  .MEASURE TRAN RTL TRIG AT=0 TARG V(Z) VAL=0.6 FALL=1
33  .MEASURE TRAN AVG_CUR AVG I(C1) FROM 0 to 'RTL'
34  .MEASURE TRAN AVG_PWR AVG P(C1) FROM 0 to 'RTL'
35
36  .END
```

## Explanation

- DRAM.sp uses input data from file input\_data.txt to run sweep analysis on DRAM with varying levels of temperature, width, and capacitance and logs it's result.

## Python scripting files

### generate\_input.py

- Run this file to generate the input data to do the sweep analysis with

- This file will create a file called “input\_data.txt”, which DRAM.sp will use to do sweep analysis

```

Lab4 > generate_input.py
1  with open('input_data.txt', 'w') as file:
2      file.write(".DATA mydata\n")
3      file.write("+ TEMP WIDTH CAP\n")
4      temp_list = [25, 85]
5      width_list = list(range(120, 301, 60)) # stops at 301 to include 300
6      cap_list = [0.01] + [8 ** (0.1 * i) for i in range(1, 11, 1)]
7      for temp in temp_list:
8          for width in width_list:
9              for cap in cap_list:
10                 file.write(str(temp) + " " + str(width) + "n " + str(cap) + "f\n")
11         file.write(".ENDDATA")

```

## Explanation

This file just generates different combinations of input condition by using for loops, and outputs it in a .txt file.

## organize\_output.py

- Run this file after you’ve ran the sweep analysis in DRAM.sp and saved the output in a file called “output.lis”
- This file reads “output.lis”, and “input\_data.txt”, and generates a new file “output\_data.txt” which visualizes the result of the sweep analysis in a nice and readable way



```

Lab4 > organize_output.py
1  from collections import deque
2
3  # The final file, line by line
4  final_result = []
5
6  with open('output.lis', 'r') as file:
7      with open('input_data.txt', 'r') as input_data:
8          # Read in the input data in order
9          for line in input_data:
10             if len(line) != 0 and line[0] != '.' and line[0] != '+' and line[0] != "\n":
11                 final_result.append(line[:-1])
12
13     # Read in data
14     counter = 0
15     # Have a buffer, because rtl, average power and current are usually within 5 lines of "job finished"
16     buffer = deque()
17     for _ in range(5):
18         buffer.append("")
19     for line in file:
20         # If key line "job concluded" is encountered, look into buffer to get the average currents and such
21         if "job concluded" in line:
22             while len(buffer) != 0:
23                 temp = buffer.popleft()
24                 temp_list = temp.strip().split(" ")
25                 hot_words = ["rtl=", "avg_cur=", "avg_pwr="]
26                 if len(temp_list) > 1 and temp_list[0] in hot_words:
27                     final_result[counter] += (" " + temp_list[1])
28                 counter += 1
29             # Repopulate the buffer
30             for _ in range(5):
31                 buffer.append("")
32             buffer.append(line)
33             buffer.popleft()
34
35     # Update final_result to add in start and finish
36     final_result = [".DATA mydata", "+ TEMP WIDTH CAP RTL AVG_CUR AVG_POWER"] + final_result + [".ENDDATA"]
37
38     # Write the data out
39     with open("output_data.txt", 'w') as file:
40         for line in final_result:
41             file.write(line + "\n")

```

## Explanation

This file reads “output.lis” and “input\_data.txt” to generate “output\_data.txt” which a readable output file with all the results.

- I used a buffer method because I realized the RTL, average power, and average current are always 5 lines before a line that contains “job concluded”. So I used that fact to read in those data from “output.lis”

## How to use

This program basically runs a sweep analysis using HSPICE on a DRAM cell using differing combinations of temperature, width, and capacitance to find out what their resulting RTL, average power, and average current is.

In order to run this program do:

1. `python3 generate_input.py`
2. `hspice -i DRAM.sp > output.lis`
3. `python3 organize_output.py`

Then you can find the output in the file: "output\_data.txt"

### **Explanation:**

(1) generates the combinations of the vary temperature, width, and capacitance conditions. (2) Runs the hspice program on those combinations and logs it in output.lis file. (3) Reads the output files and organizes the output in a readable manner in "output\_data.txt"